SCADA

List of Practical's

1	**Introduction to Components of IoT**
2	**Blinking LEDs**
3	**Interfacing LED and Switch**
4	**Stepper Motor Connection**
5	**Simulation of Traffic Signal**

Blinking LED

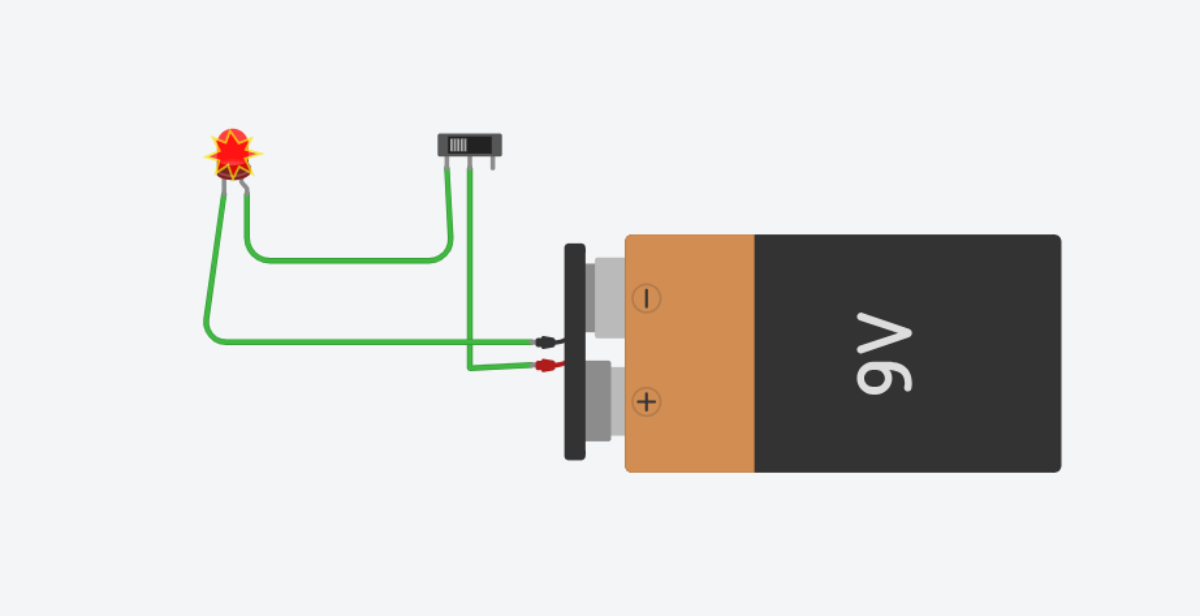

3 Interfacing LED and Switch

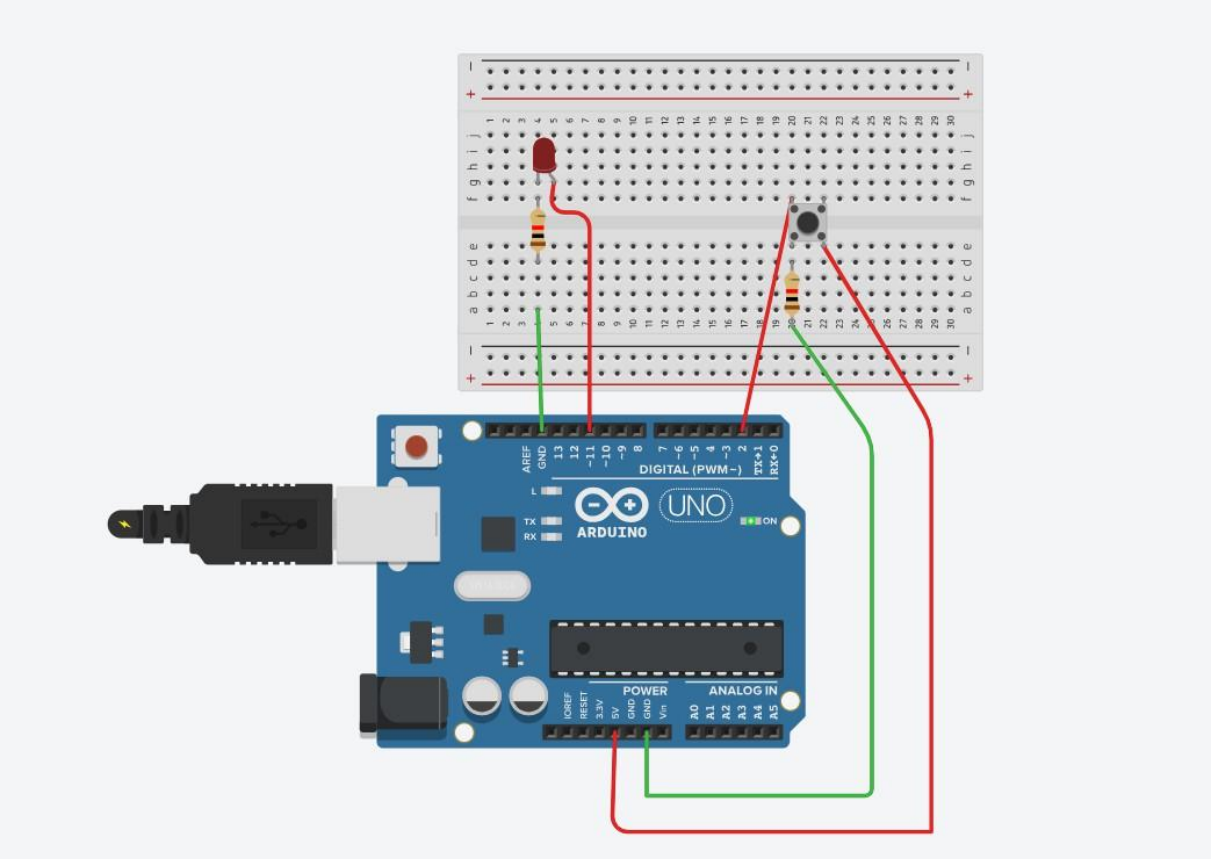

Code

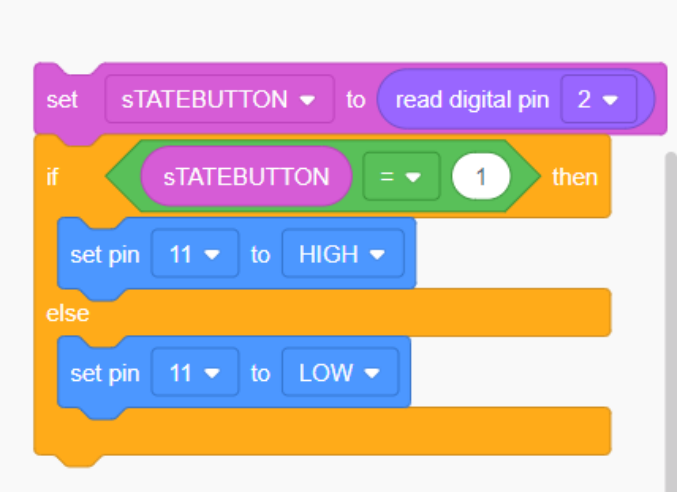

4 Stepper Motor Connection

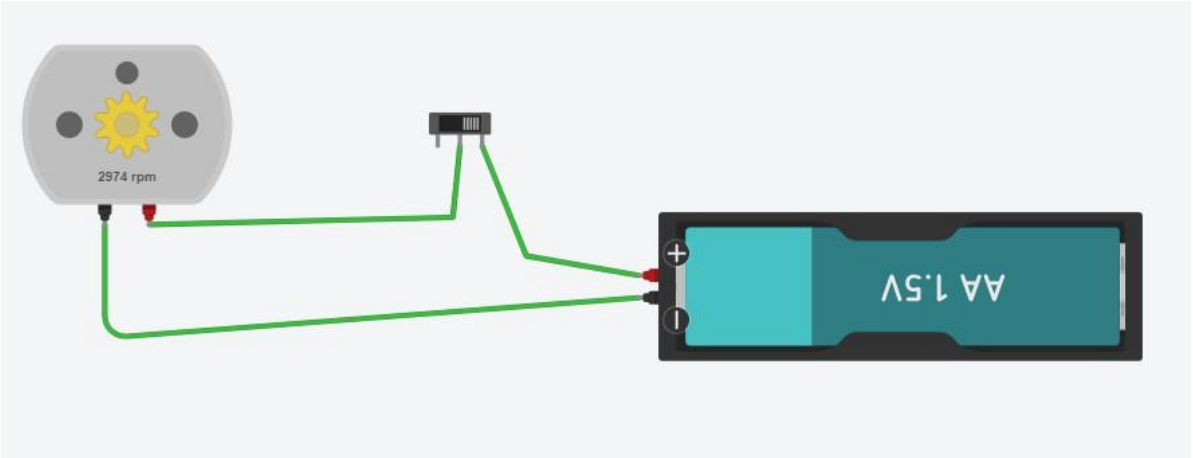

5. Simulation of Traffic Signals

Circuit diagram

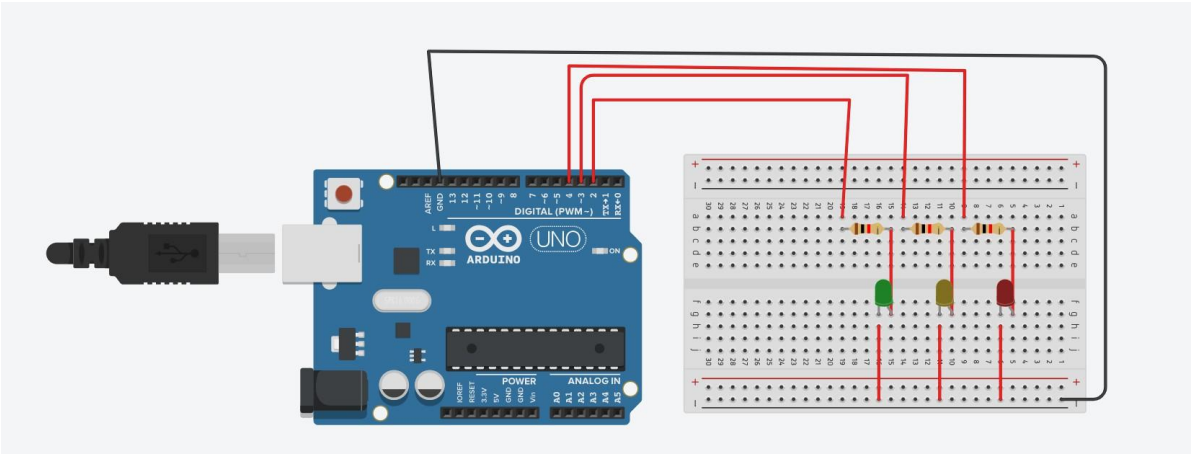
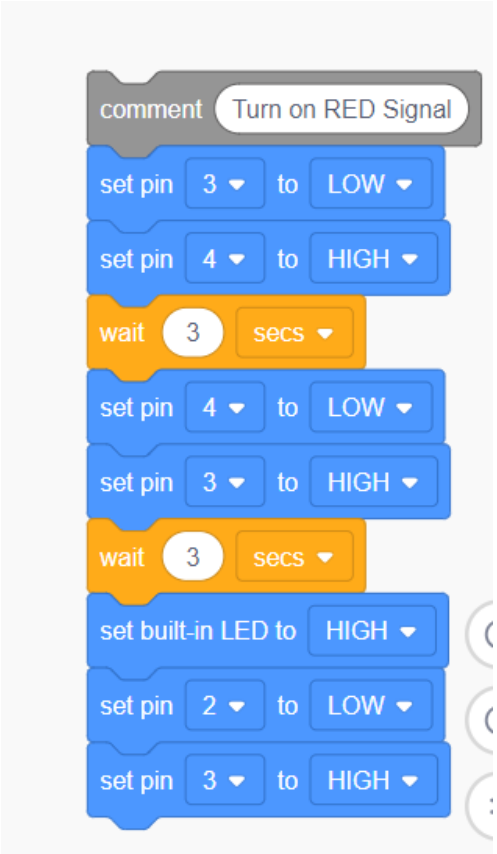
Code: